

1. **APPARATUS:** 500 cm³ beaker, water, thermometer, 100 g mass, stirrer, measuring cylinder (100 cm³), pair of tongs and Bunsen burner.

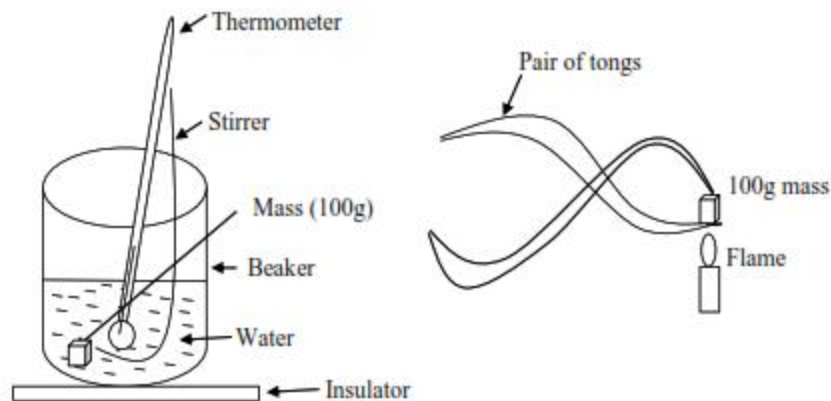


Figure 1

PROCEDURE

Using a measuring cylinder, measure 100cm³ of water into the beaker. Record this volume as V . Measure and record the initial temperature of the water t . Calculate the mass of the water M using the formula: $\text{Mass} = \text{density} \times \text{volume}$. Where density of water = 1 gcm⁻³. Using a pair of tongs, hold the 100g mass in the flame of a Bunsen burner for 4 minutes. Quickly transfer the hot 100g mass into the beaker of water. Stir gently and record the highest temperature t_1 .

$$\text{Evaluate } T = t_1 - t.$$

Empty the content of the beaker and repeat the procedure above for values of $V = 150\text{cm}^3$, 200cm^3 , 250cm^3 and 300cm^3 . Tabulate your readings.

- (i) Plot a graph with M on the vertical axis and T on the horizontal axis.
 - (ii) Determine the slope S of the graph.
 - (iii) Evaluate $K = \frac{50}{S}$
- (b)
- (i) When the bulb of a thermometer is placed in a beaker of hot water, the level of mercury first falls and then rises gradually. Explain this observation.
 - (ii) A solid of mass 100g at a temperature of 90°C is placed in 100g of water at 20°C in a container of negligible heat capacity, if the final steady temperature is 60°,

calculate the specific heat capacity of the solid. (Specific heat capacity of water = $4.2 \times 10^3 \text{ J kg}^{-1} \text{ K}^{-1}$)

[Total = 10 marks]

2. **APPARATUS:** Length of resistance wire **AB**, power source (3.0 V), key, ammeter, voltmeter and jockey.

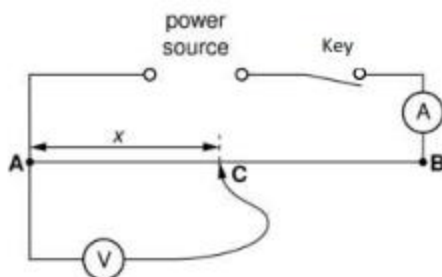


Figure 2

PROCEDURE

- Place the sliding contact **C** on the resistance wire **AB** at a distance x from **A**, where $x = 0.100 \text{ m}$.
- Record the value of x as in the Table below.
- Switch on. Using the voltmeter, measure the potential difference (V) across the wire between **A** and **C**. Record the value of V .
- Using the ammeter, measure the current I in the wire. Record the value of I .
- Take the sliding contact away from the wire **AB** and switch off.
- Calculate the resistance R of the section **AC** of the wire using the equation $R = \frac{V}{I}$
- Record R in the table.

x/m	V/V	R/Ω

- (h) Repeat steps (a) to (g) with the sliding contact at distances of $x = 0.300$ m, 0.500 m, 0.700 m and 0.900 m from A.
- (i) Plot a graph of R / Ω (y -axis) against x / m (x -axis).
- (j) Within the limits of experimental accuracy, what do you conclude about the variation of resistance with distance along the wire? Justify your conclusion with reference to your graph.
- (k) Using your graph, determine a value for the resistance R when the length $x = 0.750$ m. Show clearly on your graph how you obtained the necessary information.

[Total = 10 marks]